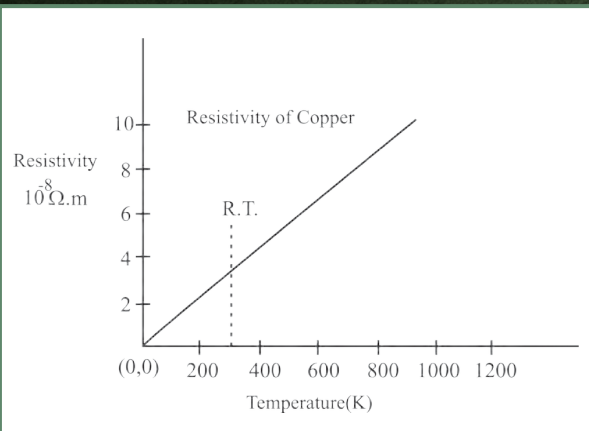


ELECTRIC CURRENT THROUGH CONDUCTOR


Chap-11

VARIATION OF RESISTANCE WITH TEMPERATURE

- Resistivity of A MATERIAL VARIES with TEMPERATURE
- Fig. shows the VARIATION of resistivity of copper AS A function of temperature (K)
- It CAN be seen THAT the VARIATION is LINEAR over A CERTAIN RANGE of temperatures
- Such A LINEAR RELATION CAN be expressed AS, $\rho = \rho_0[1 + \alpha(T - T_0)]$
- where T is the chosen reference temperature AND ρ is the resistivity AT the chosen TEMPERATURE




ELECTROMOTIVE FORCE (EMF)

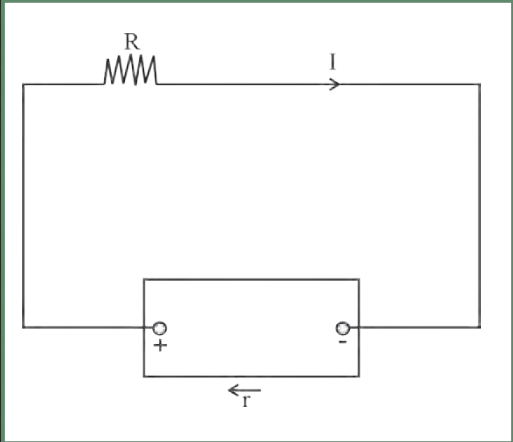


- When CHARGES flow through A CONDUCTOR, A POTENTIAL difference HAS to be ESTABLISHED between the two ends of the conductor
- For A STEADY flow of CHARGES, this POTENTIAL difference is required to be MAINTAINED ACROSS the two ends of the conductor, the terminals
- There is A device THAT does so by doing work on the CHARGES, thereby MAINTAINING the POTENTIAL difference is called battery.
- The work done or energy spent per unit charge by battery to complete one round of close circuit is called electromotive force (EMF) denoted by E
- Example of source of EMF, Power cells, BATTERIES, SOLAR cells, fuel cells, AND even GENERATORS ETC.
- Fig. shows A CIRCUIT with AN emf (E) device with internal resistance r AND A resistor R .
- Here, the emf device keeps the positive TERMINAL (+) AT A higher electric POTENTIAL THAN the NEGATIVE TERMINAL (-).
- Now suppose THAT A CHARGE dq flows through the cross section of conductor of the circuit in time dt
- The device must do work dw on the CHARGE dq , to flow from path of circuit and to maintain this flow, device must have to be doing the work.
- Thus we define the emf of the emf device $E =$
- The SI unit of emf is joule/coulomb(J/C) or volt (V)

CURRENT PASSING THROUGH CLOSE CIRCUIT

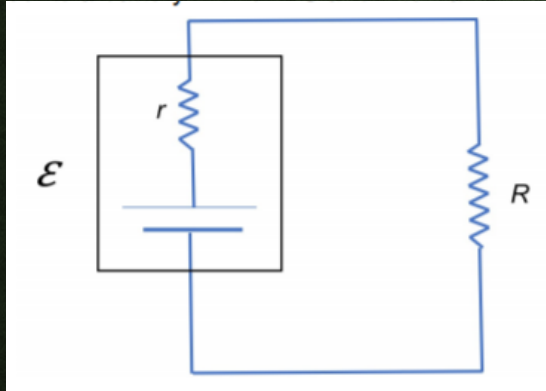

- In A REAL emf device, there is AN INTERNAL RESISTANCE to the motion of CHARGE CARRIERS
- If such A device is not connected in A CIRCUIT, there is no current through it and the emf is EQUAL to the POTENTIAL difference ACROSS the two terminals of the emf device.
- If A current (I) flows through AN emf device, there is AN INTERNAL RESISTANCE (r) AND the emf (E) differs from the POTENTIAL difference ACROSS its two TERMINALS (V) i.e. $V = E - (I)(r)$
- The NEGATIVE sign is due to the FACT THAT the current I flows through the emf device from the NEGATIVE TERMINAL to the positive TERMINAL
- By the APPLICATION of Ohm's LAW, $V = IR$
- HENCE, $IR = E - (I)(r)$
- $IR + Ir = E \quad \Rightarrow I =$
- Thus, the MAXIMUM current THAT CAN be DRAWN from the emf device is when $R = 0$, i.e.

CELLS IN SERIES

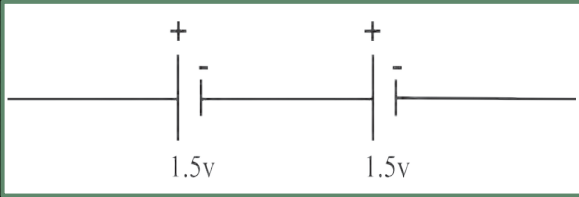

- In A SERIES COMBINATION, cells ARE connected in single ELECTRICAL PATH, such THAT the positive TERMINAL of one cell is connected to the NEGATIVE TERMINAL of the next cell, AND so on
- The TERMINAL VOLTAGE of BATTERY/CELL is EQUAL to the sum of VOLTAGES of INDIVIDUAL cells in series
- The EQUIVALENT emf of n number of cells in series COMBINATION is the ALGEBRAIC sum of their INDIVIDUAL emf
- The EQUIVALENT INTERNAL RESISTANCE of n cells in A SERIES COMBINATION is the sum of their INDIVIDUAL INTERNAL RESISTANCE
- HENCE, TERMINAL POTENTIAL DIFFERENCE, $V = \mathcal{E} - I r$
- ADVANTAGES of cells in series:
 - 1) The cells connected in series produce A LARger RESULTANT VOLTAGE
 - 2) Cells which ARE DAMAGED CAN be EASILY identified, hence CAN be EASILY REPLACED

CELLS IN PARALLEL

- In parallel combination, positive TERMINALS of ALL the cells ARE connected together AND the NEGATIVE TERMINALS of ALL the cells ARE connected together
- In PARALLEL connection, the current is divided AMONG the BRANCHES i.e. AND AS SHOWN in fig
- Consider points AND HAVING POTENTIALS AND , respectively
- Hence, potential difference across terminal is $V = -$

$$\text{for cell } , V = - \Rightarrow =$$

$$\text{for cell } V = - \Rightarrow =$$

- But $I = + = +$

$$I = - + - = + - V$$

$$V = + - I$$


$$V = - I$$

$$= - I$$

$$=$$

$$\text{where } = \text{ and } = \text{ i.e. } = \text{ and } =$$

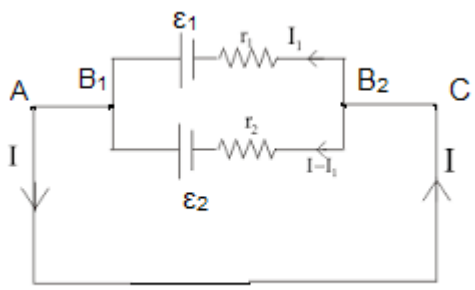- For n number of cells connected in PARALLEL, $= \text{-----}+$ and $= \text{-----}+$



ADVANTAGE AND DISADVANTAGE OF PARALLEL COMBINATION

- **ADVANTAGES of cells in PARALLEL :** For cells connected in PARALLEL in A CIRCUIT, the circuit will not BREAK open even if A CELL gets DAMAGED or open
- **DISADVANTAGES of cells in PARALLEL :** The VOLTAGE developed by the cells in PARALLEL connection CANNOT be INCREASED by INCREASING number of cells present in circuit

TYPES OF CELLS

- **Primary cell:** A PRIMARY cell CANNOT be CHARGed AGAIN. It CAN be used only once.
- E.g. Dry cells, ALKALINE cells etc.
- **Secondary cell:** The SECONDARY cell ARE RECHARGEABLE AND CAN be reused.
- The CHEMICAL REACTION in A SECONDARY cells is reversible
- E.g. LEAD ACID cell, AND fuel cell
- **Fuel cells vehicles (FCVs):** Fuel cells vehicles (FCVs) ARE electric vehicles THAT use fuel cells INSTEAD of LEAD ACID BATTERIES to power the vehicles
- Hydrogen is used AS A fuel in fuel cells
- The by- product AFTER its burning is WATER
- This is IMPORTANT in terms of reducing emission of greenhouse GASES produced by TRADITIONAL GASOLINE fueled vehicles
- The hydrogen fuel cell vehicles ARE thus more environment friendly